
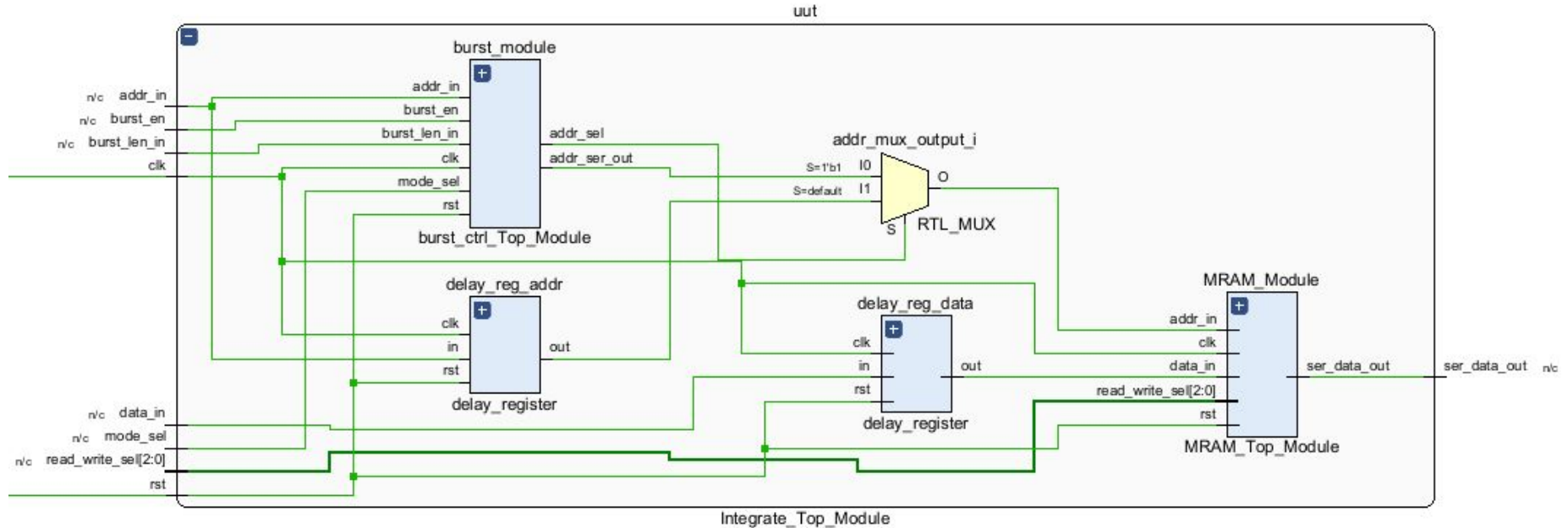


Timing analysis


Integrated Overview of Controller

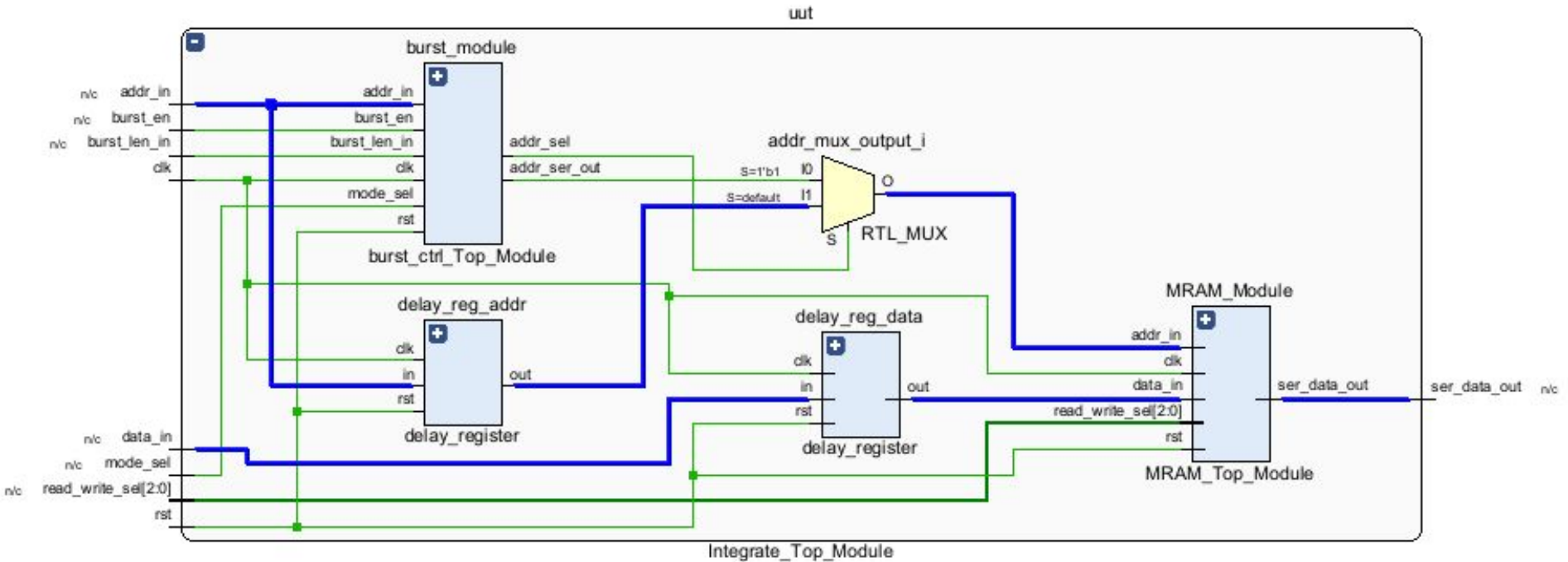

During Single Transfer / First loop of Burst Transfer




During Burst Transfer

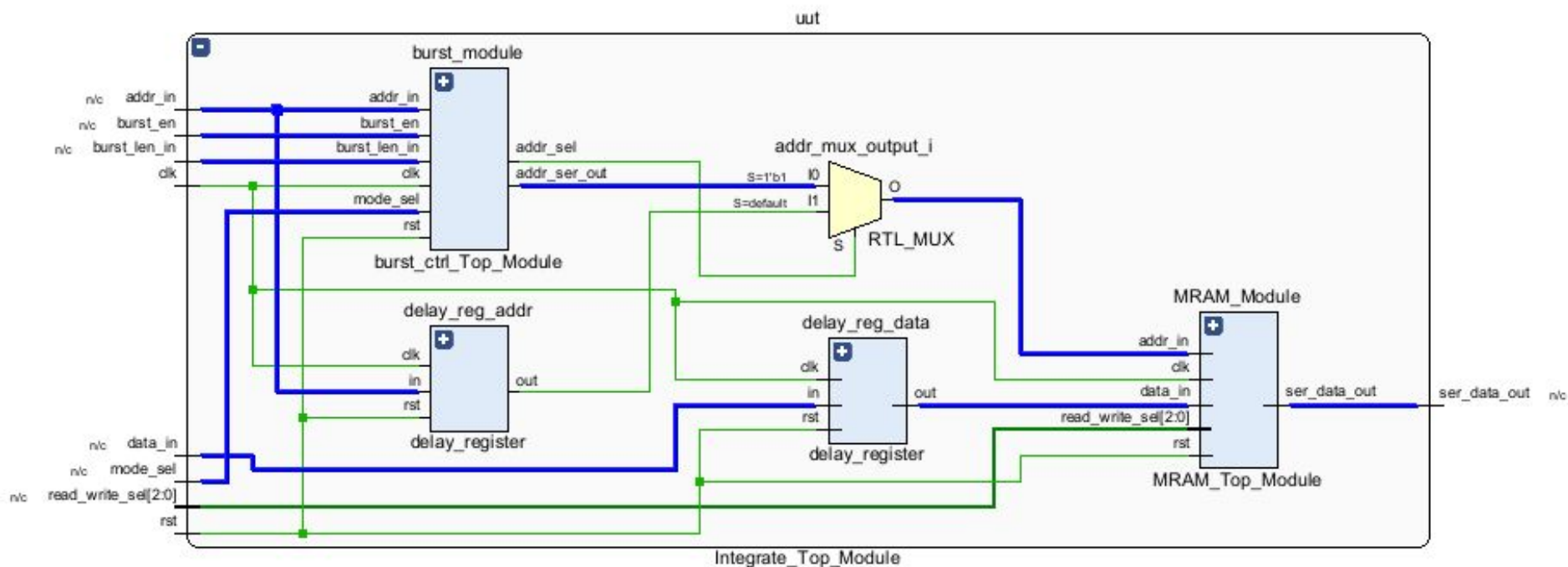


Burst Module

If Single Transfer is selected, don't do anything.


Done through setting the mux to 0.

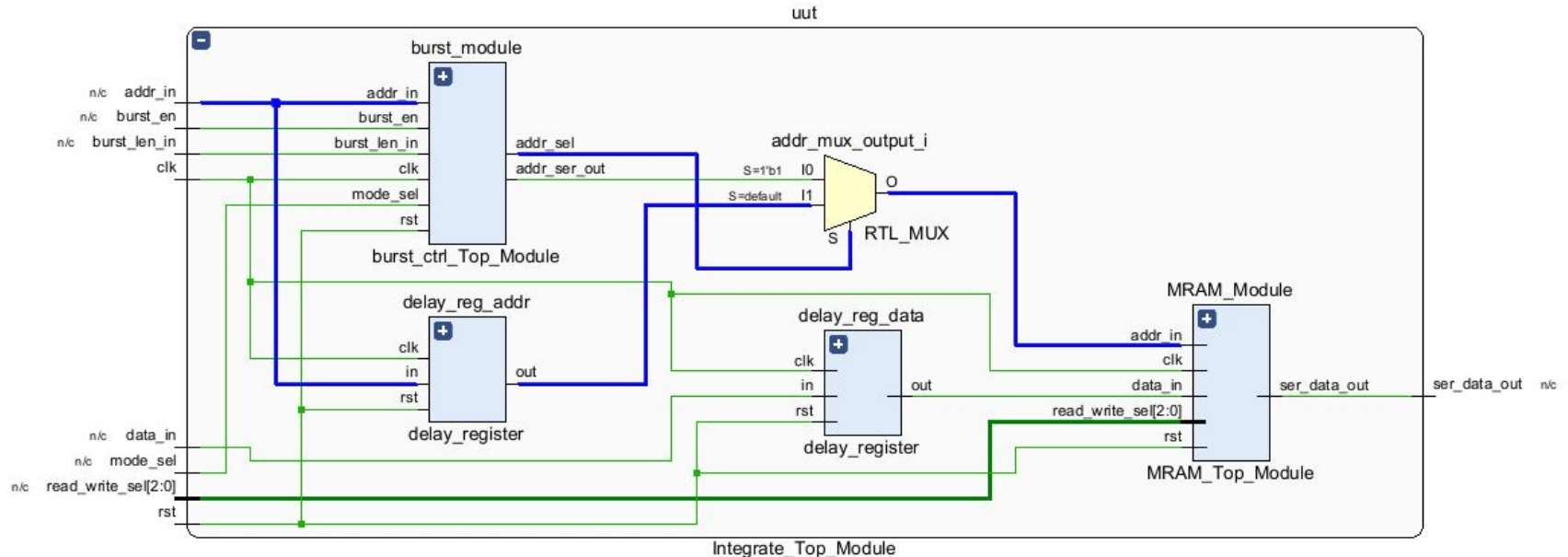


Burst Module - Burst len

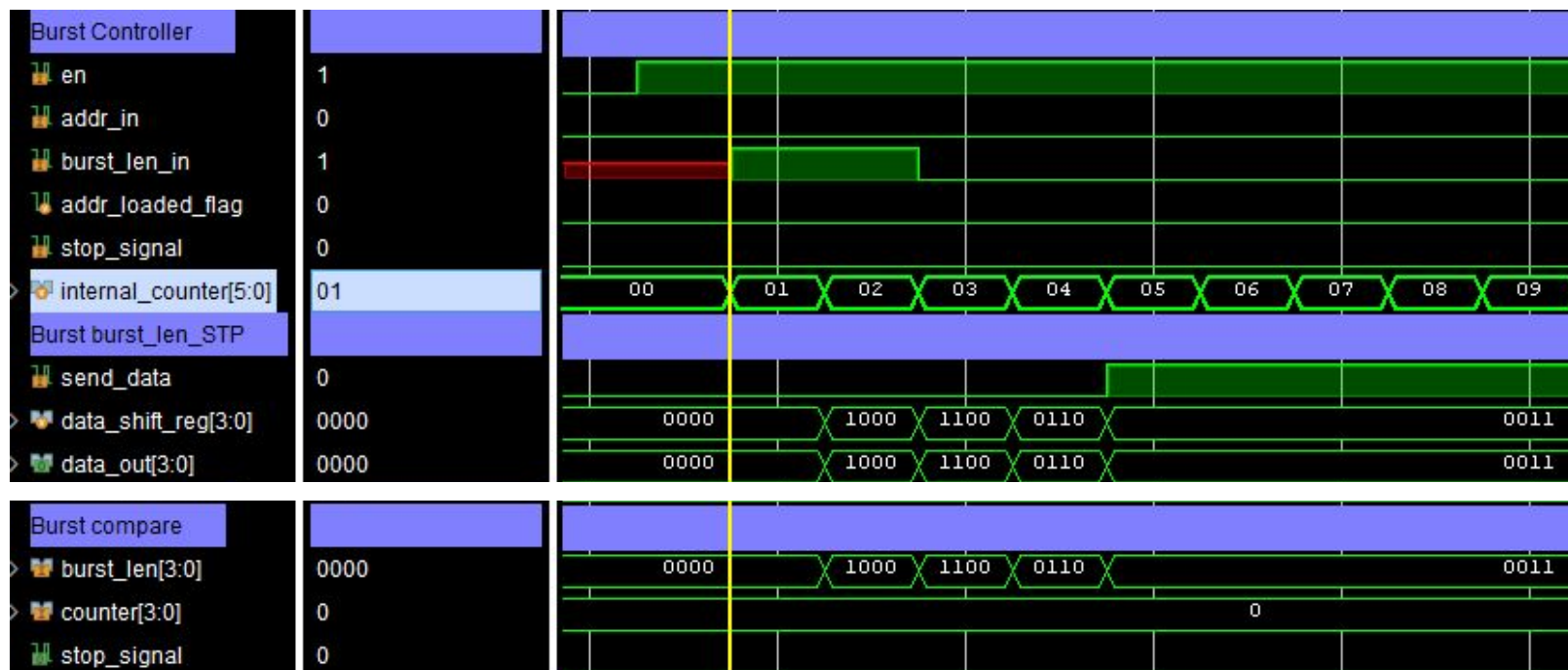

Burst Module - Initial addr

 


Burst Module - Initial addr

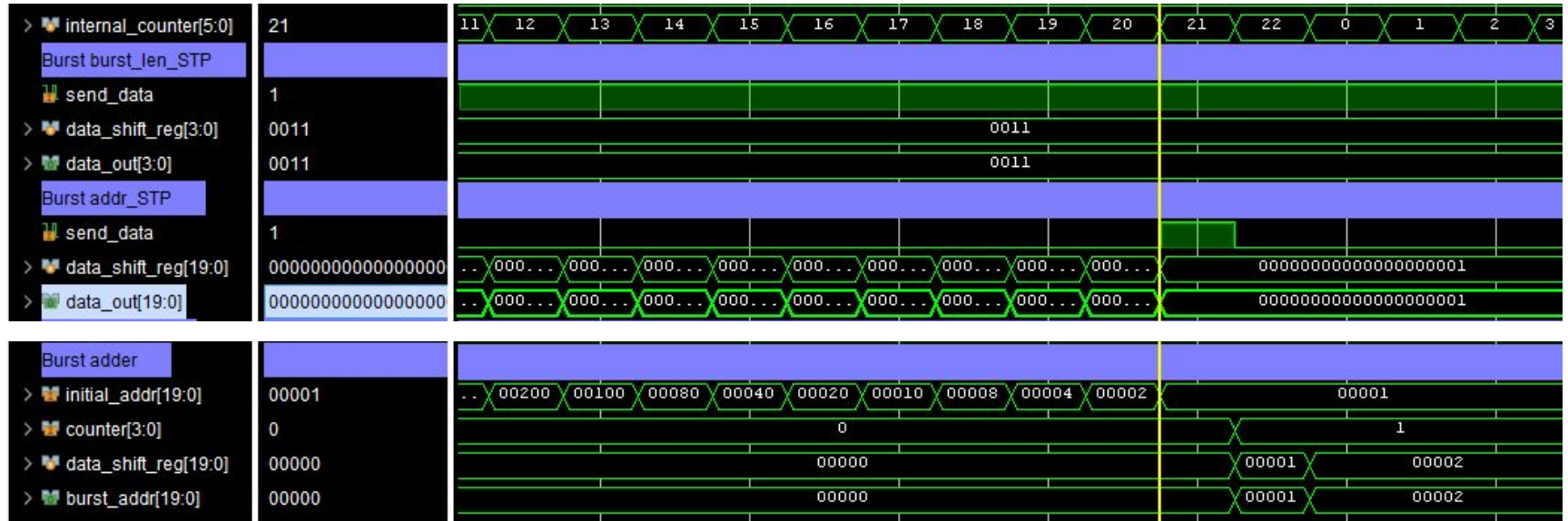

Burst Module - Initial addr

After initial addr is loaded, set the loaded flag and addr_sel(mux control)

 Addr read for the STP/PTS module starts when counter = 2




Burst Module - Adder

Takes initial addr and counter module's value and adds them tgt




Burst Module - compare module

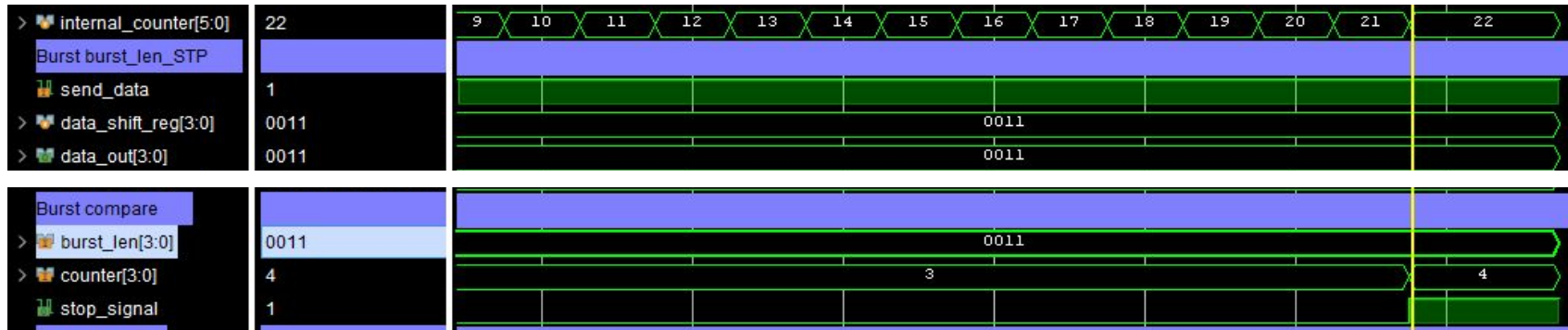
Cycle 22: When compare module detects that the counter value exceeds the burst len, assert stop signal to the burst control to stop sending address serially



Burst Module - address PTS module

 


MRAM STP/PTS module -

 

MRAM STP/PTS module - data/addr STP module (write op)

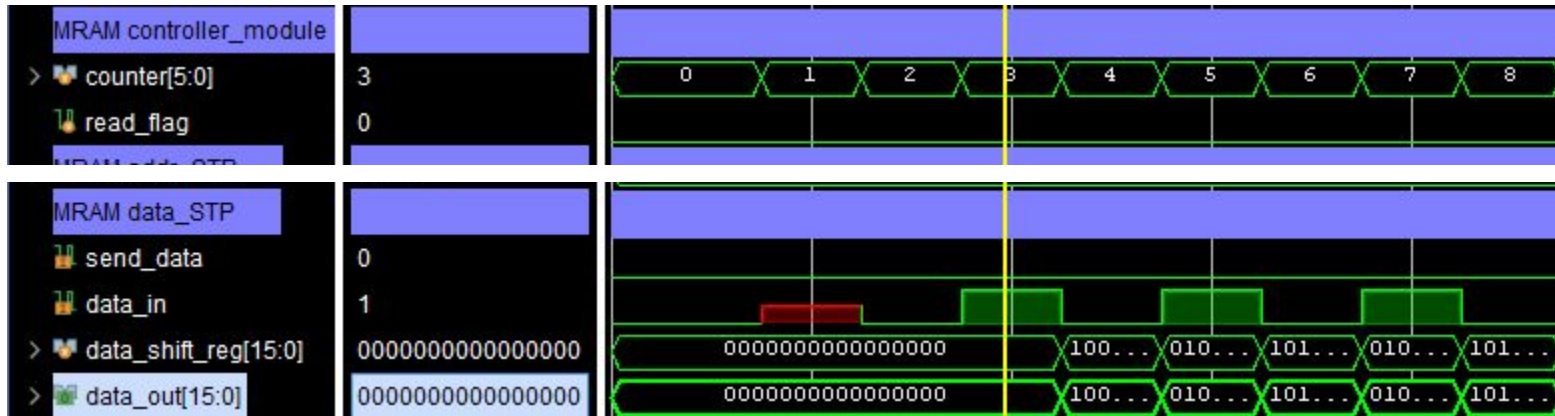At counter = 2, data gets read and takes 1 cycle to be shifted into the internal shift register




MRAM STP/PTS module - data/addr STP module (write op)

At counter = 18, data is fully in the internal shift register.

At counter = 22, addr is fully in the internal shift register.

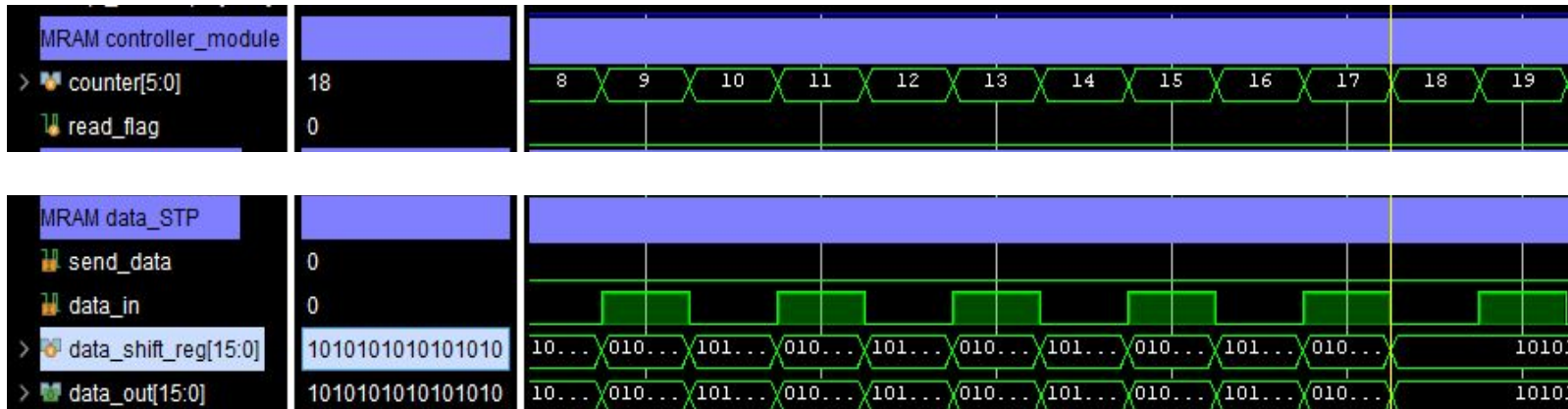Can be sent to the MRAM alongside the control signals



MRAM STP/PTS module - addr STP module (write op)

At counter = 22, signals are asserted to write to the MRAM


At counter = 0 of the next cycle, it is in the MRAM



MRAM STP/PTS module - Read operation

Data is read out in the next loop after address is provided

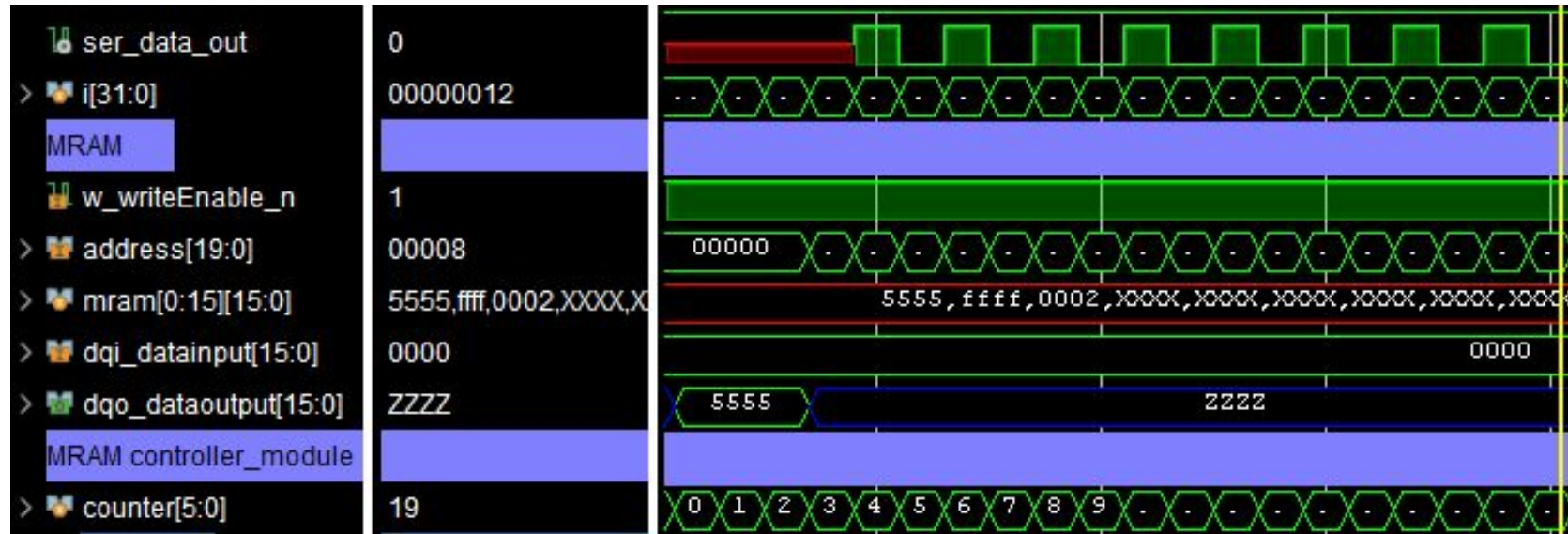Addr = 0; data in address 0 is 5555h, 0101_0101_0101_0101b. Data is output from LSB to MSB



Testbench - burst read example

```
198 //-----
199 // BURST READ
200 ○ @(posedge clk)
201 ○ rst <= 0;
202
203 ○ burst_en <= 1;
204 ○ mode_sel <= 1;
205 ○ read_write_sel <= 3'b110;
206
207 ○ @(posedge clk)
208 ○ burst_len_in <= 1;
209 ○ addr_in <= 0;
210
211 ○ @(posedge clk)
212 ○ burst_len_in <= 1;
213 ○ addr_in <= 0;
214
215 ○ for (i = 0; i < 18; i = i+1) begin
216 ○   @(posedge clk)
217 ○   addr_in <= 0;
218 ○   burst_len_in <= 0;
219 ○ end
220
221 ○ @(posedge clk)
222 ○ @(posedge clk)
223 ○ @(posedge clk)
224
225
226 // Stall to see output
227 ○ @(posedge clk)
228 ○ for (i = 0; i < 69; i = i+1) begin
229 ○   @(posedge clk)
230 ○   addr_in <= 0;
231 end
```


Control signals

Burst len = 3


Addr = 0

Stall to see output

MRAM	
w_writeEnable_n	1
> address[19:0]	00008
▼ mram[0:15][15:0]	5555,fff,0002,X000,X
> [0][15:0]	5555
> [1][15:0]	fff
> [2][15:0]	0002

 

Testbench - burst read example

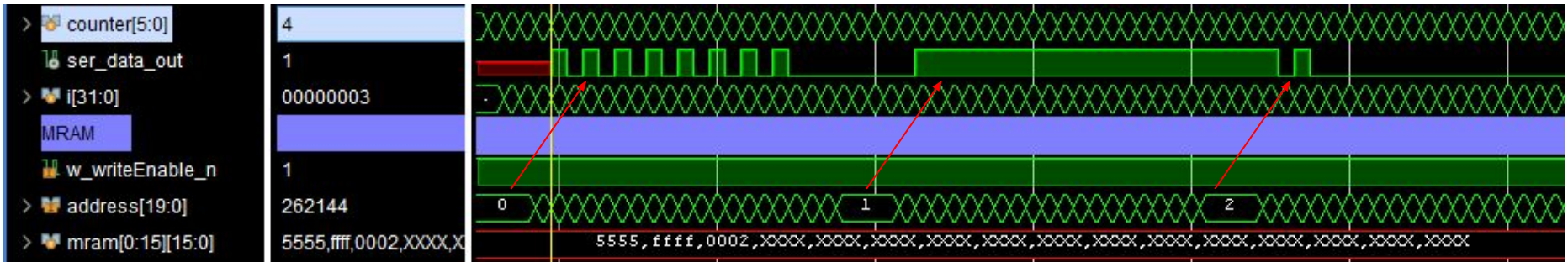

Integrated module summary

1 loop consists of 23 cycles (0-22)

Writing:

- Takes 23 cycles

Reading:

- Takes 23 cycles to provide address
- Data is output on the next loop, cycle 4 to 19